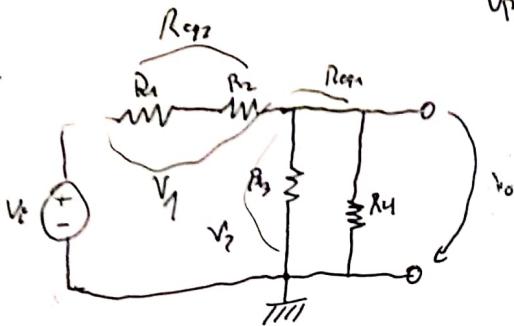


(SE)

Grafão 1.

①



$$V_{R3} = V_{R4}$$

$$V_c = 12 \text{ V}$$

$$R_1 = 470 \Omega$$

$$R_3 = 2.2 \text{ k}\Omega$$

$$R_2 = 560 \Omega$$

$$R_4 = 1.8 \text{ k}\Omega$$

$$\frac{1}{R_{eq1}} = \frac{1}{R_3} + \frac{1}{R_4} \Leftrightarrow \frac{1}{R_{eq1}} = \frac{1}{990} \Leftrightarrow R_{eq1} = 990 \Omega$$


$$R_{eq2} = R_1 + R_2 = 1030 \Omega$$

$$12 = I(1030 + 990) \Leftrightarrow I = \frac{12}{2020} = 0,00594 \text{ A}$$

$$V_1 = 1030 \times 0,00594 = 6,1182$$

$$V_2 = 12 - 6,1182 = 5,8818$$

②

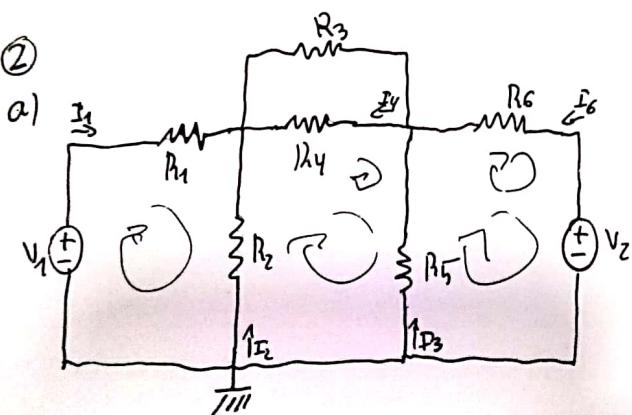

$$\begin{aligned}
 V_1 &= 10 \text{ V} & V_2 &= 5 \text{ V} \\
 R_1 &= 1 \Omega & R_2 &= 560 \Omega \\
 R_3 &= 22 \Omega & R_4 &= 470 \Omega \\
 R_5 &= 100 \Omega & R_6 &= 1 \text{ k}\Omega
 \end{aligned}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_4} + \frac{1}{R_3} \Leftrightarrow R_{eq} = 149,85 \Omega$$

$$-10 + 1000I_1 - 560I_2 = 0$$

$$5 + 100I_3 - 1000I_6 = 0$$

$$650I_2 - 149,85I_4 - 100I_3 = 0$$

$$I_1 + I_2 + I_4 = 0 \Leftrightarrow I_4 = -(I_1 + I_2)$$

$$I_6 - I_4 + I_3 = 0$$

$$I_1 \approx 0,005 \text{ A}$$

$$I_2 = 0,00306 \text{ A}$$

$$I_3 = -0,0093 \text{ A}$$

$$I_6 = 0,00407 \text{ A}$$

$$I_4 = 0,00523 \text{ A} //$$

$$c) V_{R1} = V_1 - V_{R2} = 10,09 - 1,12 = 8,97 \text{ V}$$

$$V_{R6} = V_2 - V_{R5} = 5,04 - 1,11 = 3,93 \text{ V}$$

$$I_1 = \frac{8,97}{1000} = 0,00897 \text{ A}$$

$$I_6 = \frac{3,93}{1000} = 0,00393 \text{ A}$$

$$Ex^c 2' \\ 8,95 \quad R_1$$

$$V = R_1 I \Leftrightarrow I = \frac{V}{R}$$

$$3,92 \quad R_2$$


$$I = \frac{8,95}{1000} = 0,00895$$

$$I_e = \frac{3,92}{1000} = 0,00392$$

$$c) V_{R_2} = 1,12 \quad V_{R_5} = 1,11 \quad (\Omega)$$

$$V_1 = 10,09 \quad V_2 = 5,04 \quad (V)$$

Ex 3.

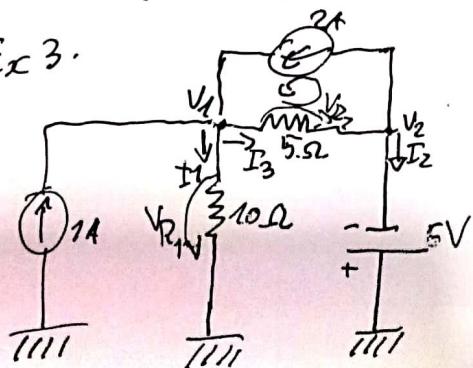

$$\begin{aligned} V_1: & 1 + 2 - I_1 - I_2 = 0 \quad \Leftrightarrow I_1 + I_2 = 3 \\ V_2: & I_2 - I_3 - 2 = 0 \quad \Leftrightarrow I_3 - I_2 = 2 \end{aligned}$$

$$2 + 5I_3 = 0 \Leftrightarrow 5I_3 = -2 \Leftrightarrow I_3 = -\frac{2}{5} A$$

$$V_{R_1} = 10 \times \frac{12}{5} = 24V$$

$$I_2 = -\frac{2}{5} - 2 = -\frac{12}{5} A$$



$$V_{R_2} = 5 \times \left(-\frac{2}{5}\right) = -2 V$$

$$I_1 = 3 - I_2 \Leftrightarrow I_1 = 3 - \left(-\frac{2}{5}\right) = \frac{17}{5} A$$


$$V_2 = -5V$$

$$V_1 = -5 + VR_2 = -7V$$

Ex 4

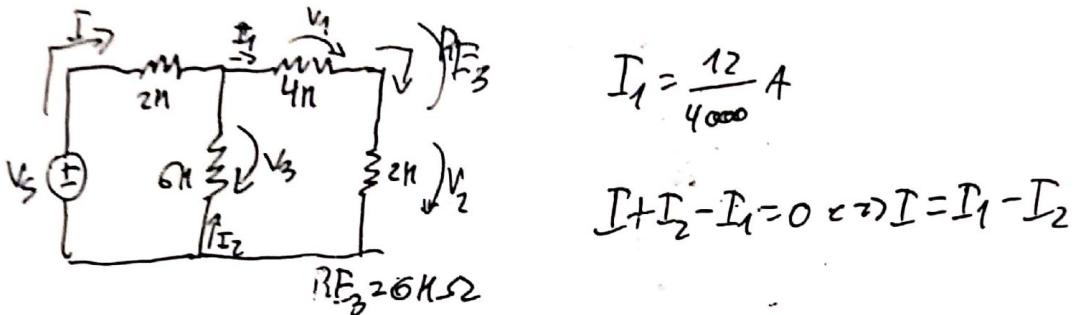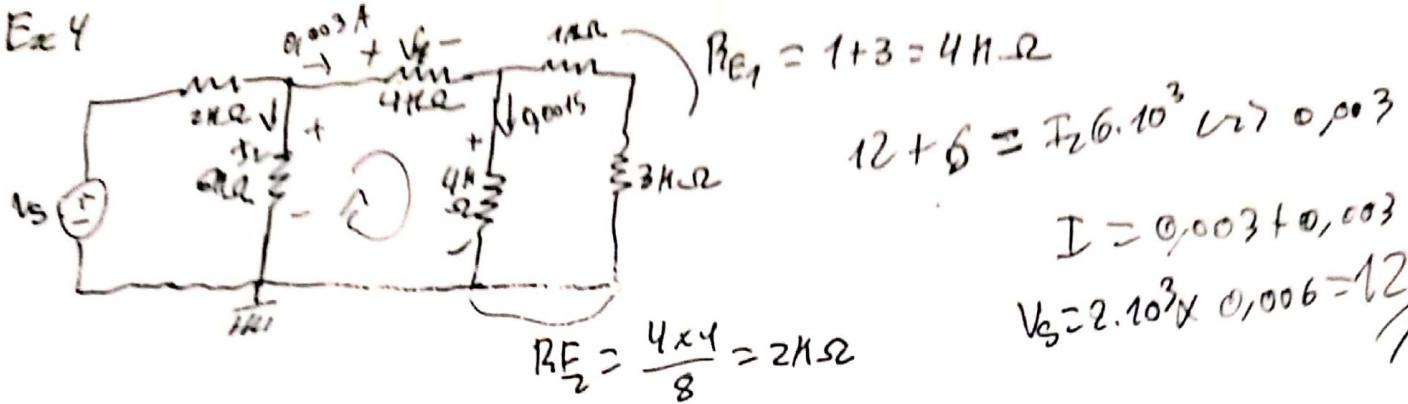

$$\text{Logo, } I_1 = I_2 = \frac{I}{2} \quad I = \frac{24}{4000} A = \frac{6}{1000} A$$

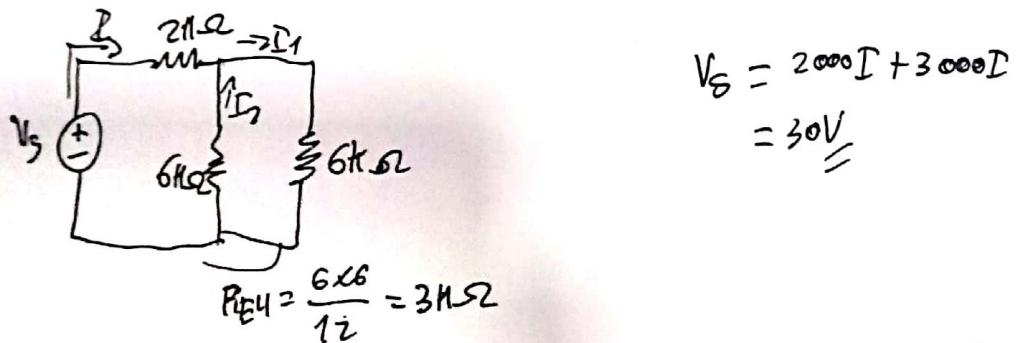

Ex 5

$$a) I_2 = g_m V_{GS} \times \frac{R_d}{R_d + R_L} \quad (\text{divisor de corrente})$$

$$V_2 = R_L \times I_2 = R_L \times g_m V_{GS} \times \frac{R_d}{R_d + R_L}$$


$$V_{GS} = V_1 \times \frac{R_g}{R_g + R_d} \quad (\text{divisor de tensão})$$

Logo,

$$V_2 = R_L \times g_m \times V_1 \times \frac{R_g}{R_g + R_d} \times \frac{R_d}{R_d + R_L} \Leftrightarrow \frac{V_2}{V_1} = R_L \times g_m \times \frac{R_g}{R_g + R_d} \times \frac{R_d}{R_d + R_L}$$

$$b) \frac{V_2}{V_1} = 10 \cdot 10^3 \times 10 \cdot 10^{-3} \times \frac{9 \cdot 10^6}{9 \cdot 10^6 + 1 \cdot 10^6} \times \frac{50 \cdot 10^3}{50 \cdot 10^3 + 10 \cdot 10^3} = 75 \parallel$$

Fr 6.

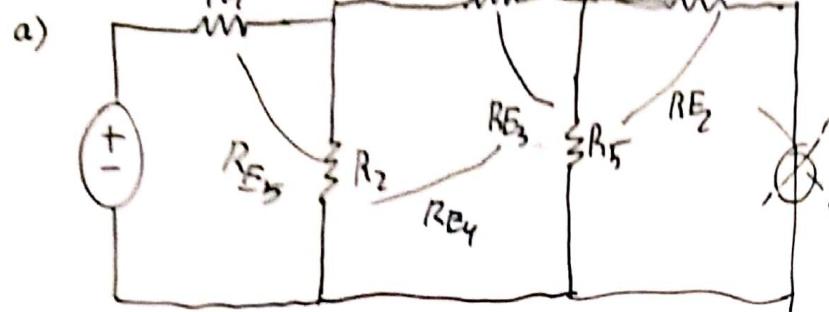

$$RE_1 = \frac{220 \times 470}{220 + 470} = 149,85 \Omega$$


$$RE_3 = 90,90 \Omega + 149,85 \Omega = 240,76 \Omega$$

$$RE_2 = \frac{1000 \times 100}{1100} = 90,90 \Omega$$


$$RE_4 = \frac{240,76 \Omega \times 560 \Omega}{560 + 240,76} = 168,37 \Omega$$

$$RE_5 = 1000 + 168,37 \Omega = 1168,37 \Omega$$


$$I_1 = \frac{10}{1168,37} = 0,00856 A$$

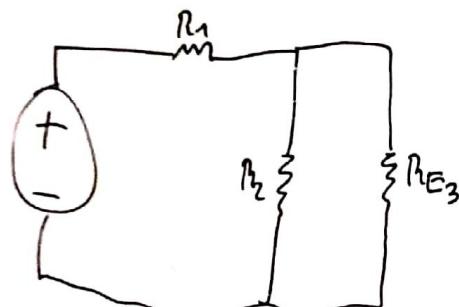
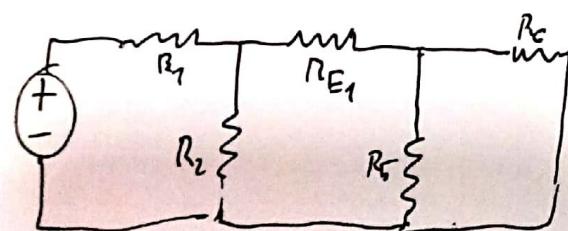
$$I_{RE_3} = I_1 \cdot \frac{R_2}{R_2 + RE_3} = 0,00856 \times \frac{560}{560 + 240,76} = 0,00599 A$$


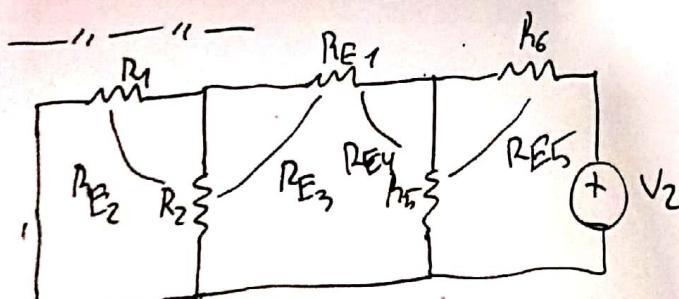
$$I_6 = 0,00599 A \times \frac{100}{1100} = 5,44 \cdot 10^{-4} A$$



$$RE_2 = \frac{1000 \times 560}{1560} = 358,97 \Omega$$


$$RE_4 = \frac{508,82 \times 100}{608,82} = 83,57 \Omega$$

$$RE_3 = 358,97 + 149,85 = 508,82 \Omega$$

$$RE_5 = 83,57 + 1000 = 1083,57 \Omega$$

$$I_6 = \frac{5}{1083,57} = 0,0046152$$
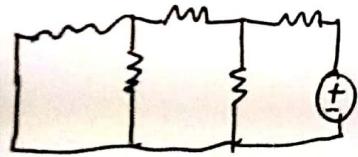
$$I_{RE_3} = 0,00461 \times \frac{100}{100 + 508,82} = 7,57 \cdot 10^{-4} A$$



$$I_1 = -7.57 \cdot 10^{-4} \times \frac{560}{1560} = -2.72 \cdot 10^{-4} A$$

$$I_1 = 0,00856 - 2.72 \cdot 10^{-4} = 0,008288 A$$

$$I_6 = 0,00461 - 5,44 \cdot 10^{-4} = 0,004066 A$$

AlgC

Pesquisabimária (cont.)

$$\text{middle} = (\text{left} + \text{right}) / 2$$

while ($\text{left} \leq \text{right}$) {


 if (...)

}

 return ...

Exemplo simples

$P_{\text{on}} \text{ (Caso}$	m casos	$X = v[i]$	$Falha$
N° de interações			
$W_I(m) = 1 + \log_2 m$			$x < v[0]$ $v[0] \leq x < v[1]$ ⋮ $x > v[n-1]$

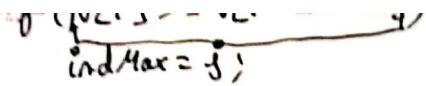

}
 if (indMax != i)
 troca (& v[i], & v[j]);

$$\sum_{i=1}^{n-1} i = \frac{n-1}{2} \times n$$

TROCAS → dependem da configuração inicial.

}
 $B_T(n) = 0$, se já ordenado

}
 $W_T(n) = (n-1)$, Mas não é o array de ordem inversa.

$P(\text{não estiver na posição certa}) = (1 - \frac{1}{n})$

$$A_T(n) = \sum_{n=2}^m (1 - \frac{1}{n}) \times 1 = m - \ln m$$

↑ inversa.


SE

Guiaço 1.

Ex 5

Thévenin


c)

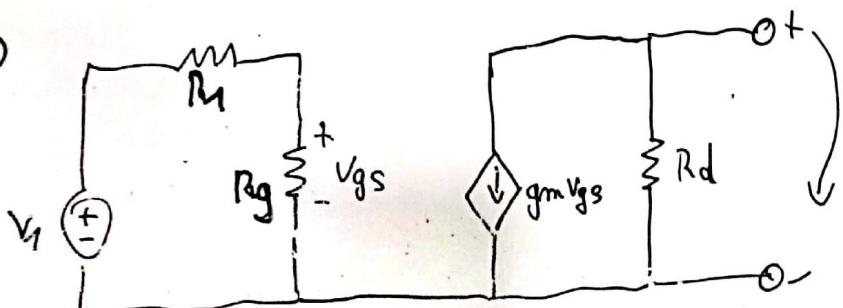

$$V_0 = g_m V_{gs} \times (-R_d) = -g_m \times \frac{V_1 R_g R_d}{R_g + R_d}$$

$$V_{gs} = V_1 \times \frac{R_g}{R_g + R_d}$$


Norton

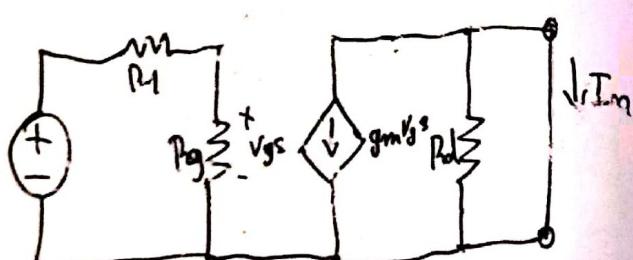

$$I_m = g_m V_{gs}$$


$$V_{gs} = V_1 \times \frac{R_g}{R_g + R_d}$$
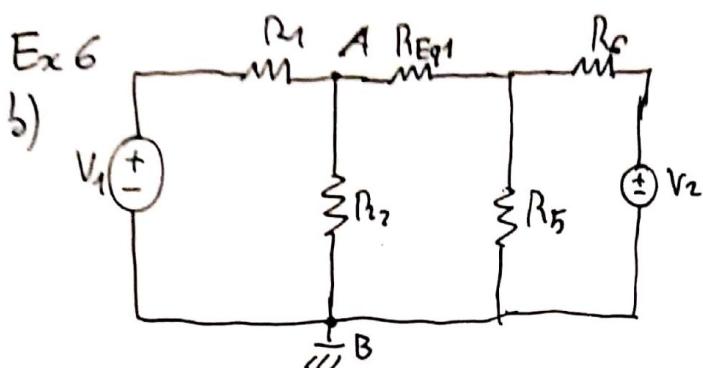
$$I_m = g_m \times \frac{V_1 R_g}{R_g + R_d}$$




$$R_{Eq1} = 144,85 \Omega$$

$$R_{Eq2} = 358,97 + 144,85 = 508,82$$

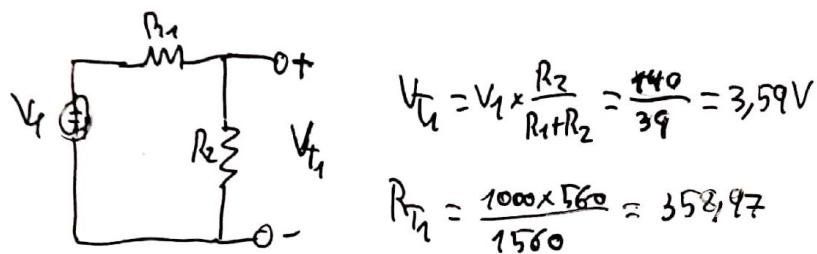


$$V_{T1} = V_1 \times \frac{R_2}{R_1 + R_2} = \frac{140}{39} = 3,59 \text{ V}$$
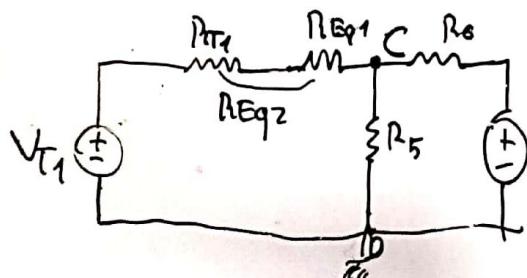
$$R_{T1} = \frac{1000 \times 560}{1560} = 358,97$$




$$V_{T2} = V_{T1} \times \frac{R_5}{R_5 + R_{Eq2}} = 0,59 \text{ V}$$
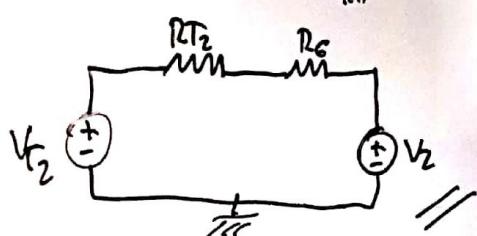
$$R_{T2} = \frac{508,82 \times 100}{100 \times 508,82} = 83,57 \Omega$$



c) $V_{R1} = 9,13 \Omega$

Ex 5 c)

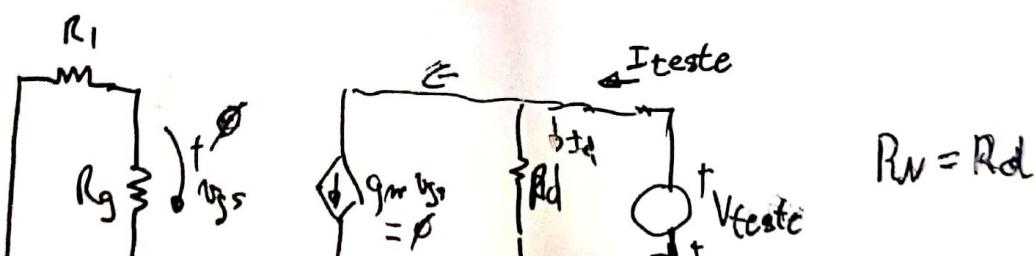

$A = 20$
 $B = 11$
 $C = 12$
 $D = 13$
 $E = 14$
 $F = 15$

$0 \rightarrow abcdef$	$\begin{array}{ccccccccc} 1 & 5 & 1 & 9 & f & e & d & c & b \\ 0 & 0 & 1 & 1 & 1 & 1 & 1 & 1 & 1 \end{array} = 0x3F$
$1 \rightarrow bc$	$\begin{array}{ccccccccc} 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 \\ 0 & 1 & 0 & 1 & 1 & 0 & 1 & 1 \end{array} = 0x06$
$2 \rightarrow abged$	$\begin{array}{ccccccccc} 0 & 1 & 0 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 0 & 1 & 1 & 0 & 1 & 1 \end{array} = 0x5B$
$3 \rightarrow Abgcd$	$\begin{array}{ccccccccc} 0 & 1 & 0 & 0 & 1 & 1 & 1 & 1 \\ 0 & 1 & 1 & 0 & 0 & 1 & 1 & 0 \end{array} = 0x4F$
$4 \rightarrow fbgc$	$\begin{array}{ccccccccc} 0 & 1 & 1 & 0 & 0 & 1 & 1 & 0 \\ 0 & 1 & 1 & 1 & 1 & 0 & 1 & 1 \end{array} = 0x66$
$6 \rightarrow afedcg$	$\begin{array}{ccccccccc} 0 & 1 & 1 & 1 & 1 & 1 & 0 & 1 \\ 0 & 1 & 1 & 0 & 1 & 1 & 0 & 1 \end{array} = 0x7D$
$5 \rightarrow afgcd$	$\begin{array}{ccccccccc} 0 & 1 & 1 & 0 & 1 & 1 & 0 & 1 \\ 0 & 1 & 1 & 0 & 1 & 0 & 1 & 1 \end{array} = 0x6D$
$7 \rightarrow abc$	$\begin{array}{ccccccccc} 0 & 1 & 0 & 0 & 0 & 1 & 1 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 1 & 1 \end{array} = 0x07$
$8 \rightarrow abcdefg$	$\begin{array}{ccccccccc} 0 & 1 & 1 & 1 & 1 & 1 & 1 & 1 \\ 0 & 1 & 1 & 0 & 0 & 1 & 1 & 1 \end{array} = 0x7F$
$9 \rightarrow abcfg$	$\begin{array}{ccccccccc} 0 & 1 & 1 & 0 & 0 & 1 & 1 & 1 \\ 0 & 1 & 1 & 1 & 0 & 1 & 1 & 1 \end{array} = 0x67$
$A \rightarrow abcefg$	$\begin{array}{ccccccccc} 0 & 1 & 1 & 0 & 1 & 0 & 1 & 1 \\ 0 & 1 & 1 & 1 & 1 & 1 & 0 & 1 \end{array} = 0x77$
$b \rightarrow cddefg$	$\begin{array}{ccccccccc} 0 & 1 & 1 & 1 & 1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 1 & 1 & 0 & 1 & 0 \end{array} = 0x7C$
$c \rightarrow adef$	$\begin{array}{ccccccccc} 0 & 0 & 1 & 1 & 1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 1 & 0 & 1 & 1 & 0 \end{array} = 0x39$
$d \rightarrow bcdeg$	$\begin{array}{ccccccccc} 0 & 1 & 0 & 1 & 1 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 & 1 & 1 & 0 & 0 \end{array} = 0x5E$
$E \rightarrow adefg$	$\begin{array}{ccccccccc} 0 & 1 & 1 & 1 & 0 & 1 & 0 & 1 \\ 0 & 1 & 1 & 1 & 1 & 0 & 1 & 0 \end{array} = 0x79$
$F \rightarrow aefg$	$\begin{array}{ccccccccc} 0 & 1 & 1 & 1 & 1 & 0 & 0 & 1 \\ 0 & 1 & 1 & 1 & 1 & 0 & 0 & 1 \end{array} = 0x71$

SE

Eccha 1.

$$R_1, R_2$$

$$1) R_{E1} = \frac{70 \times 30}{100} = 21 \Omega \quad R_{E2} = \frac{60 \times 40}{100} = 24 \Omega \quad R_{EAB} = 21\Omega + 24\Omega = 45\Omega$$

$$2) R_{E1} = \frac{18 \cdot 10^3 \times 63 \cdot 10^3}{18 \cdot 10^3 + 63 \cdot 10^3} = 14k\Omega \quad R_{ab} = 4 \cdot 10^3 + 6 \cdot 10^3 + 12 \cdot 10^3 = 22k\Omega$$

$$R_{E2} = \frac{30 \cdot 10^3 \times 15 \cdot 10^3}{30 \cdot 10^3 + 15 \cdot 10^3} = 10k\Omega$$

$$R_{E3} = 14 \cdot 10^3 + 10 \cdot 10^3 + 6 \cdot 10^3 = 30k\Omega$$

$$R_{E4} = \frac{30 \cdot 10^3 \times 20 \cdot 10^3}{30 \cdot 10^3 + 20 \cdot 10^3} = 12k\Omega$$

P1º caso - Fase de Ordenação

$$W_c(n) = \sum_{k=1}^{n-1} 2L \log_2 k \quad \leftarrow \text{Nao ha formula fechada.}$$

$$W_{\text{ordenacao}}(n) \in O(n \log n)$$

SE

condensadores

$$102 = 10 \cdot 10^2 = 1000 \mu F = 1 mF$$


$$473 = 47 \cdot 10^3 = 47000 \mu F = 47 mF$$

$$\tau = RC = 10 \times 1 mF$$

Equao 2. pt 1

1.1. a)

--- Canal 2
— Canal 1

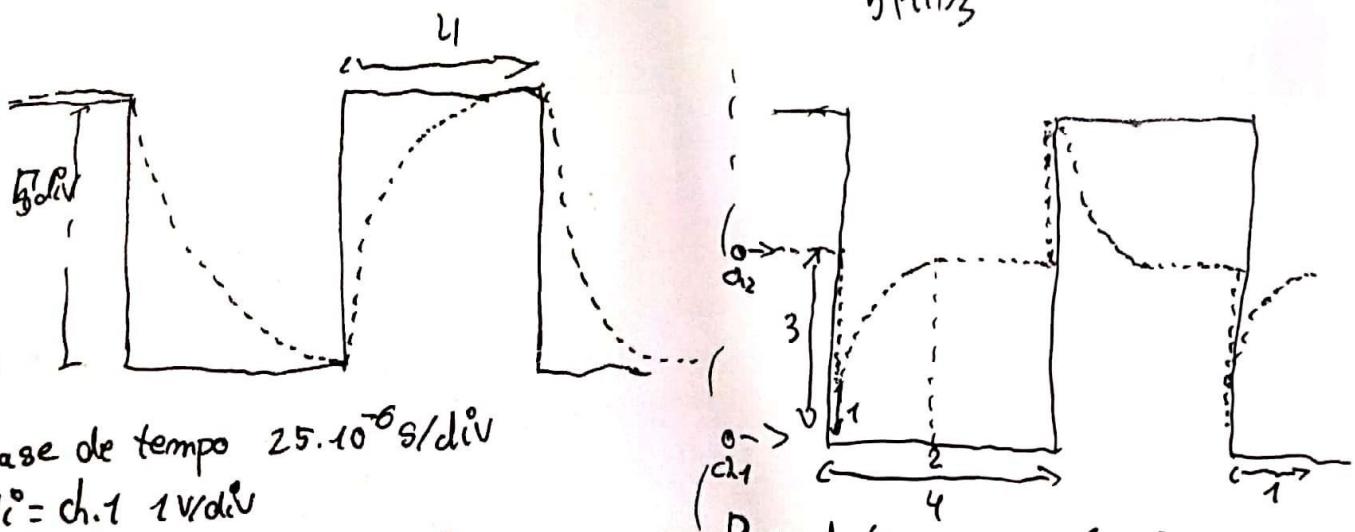



Base de tempo $25 \cdot 10^{-6} s/div$

$V_i = \text{ch.1 } 1V/div$

Ponta x: 1x Acopl: CC

$V_o = \text{ch.2 } 2V/div$

Ponta x: 1x Acopl: CC

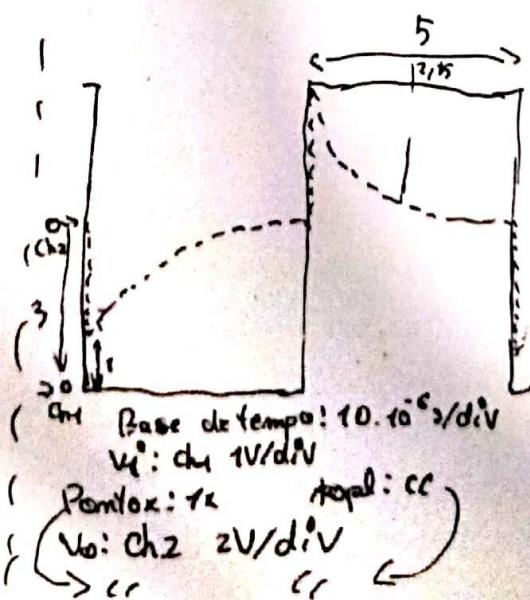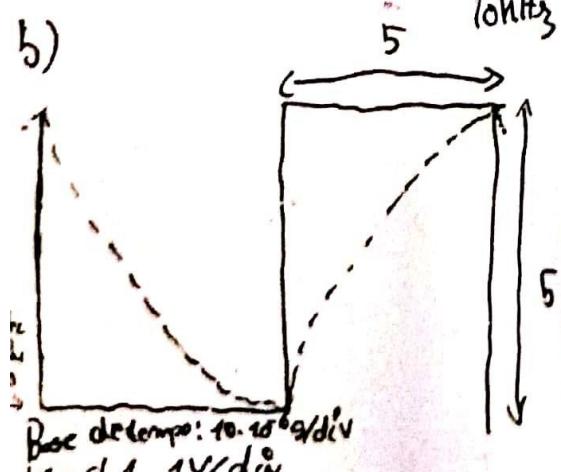

Wcondenador (m) e Wcondensador

SE




Canal encadeado

$$102 = 10 \cdot 10^2 = 1000 \mu F = 1 mF$$
$$473 = 47 \cdot 10^3 = 47000 \mu F = 47 mF$$

$$\tau = RC = 10k \times 1 mF$$


Solução 2. pt 1

1.1. a)

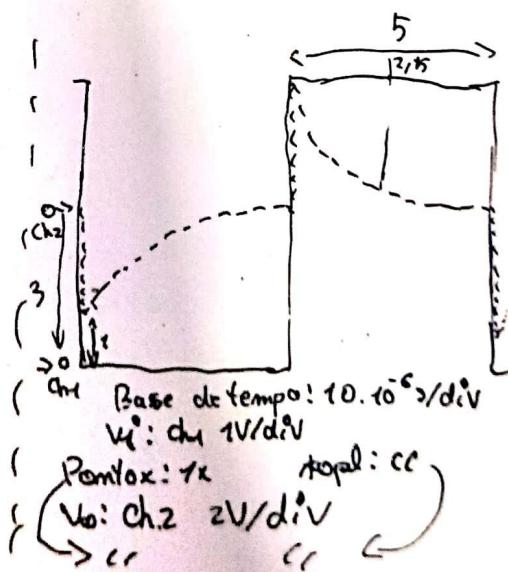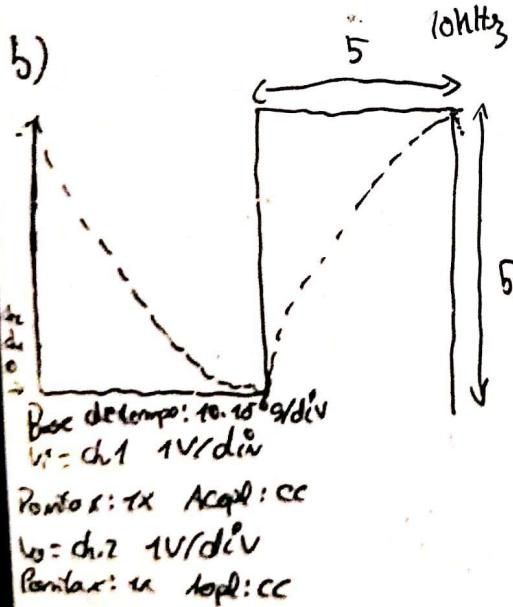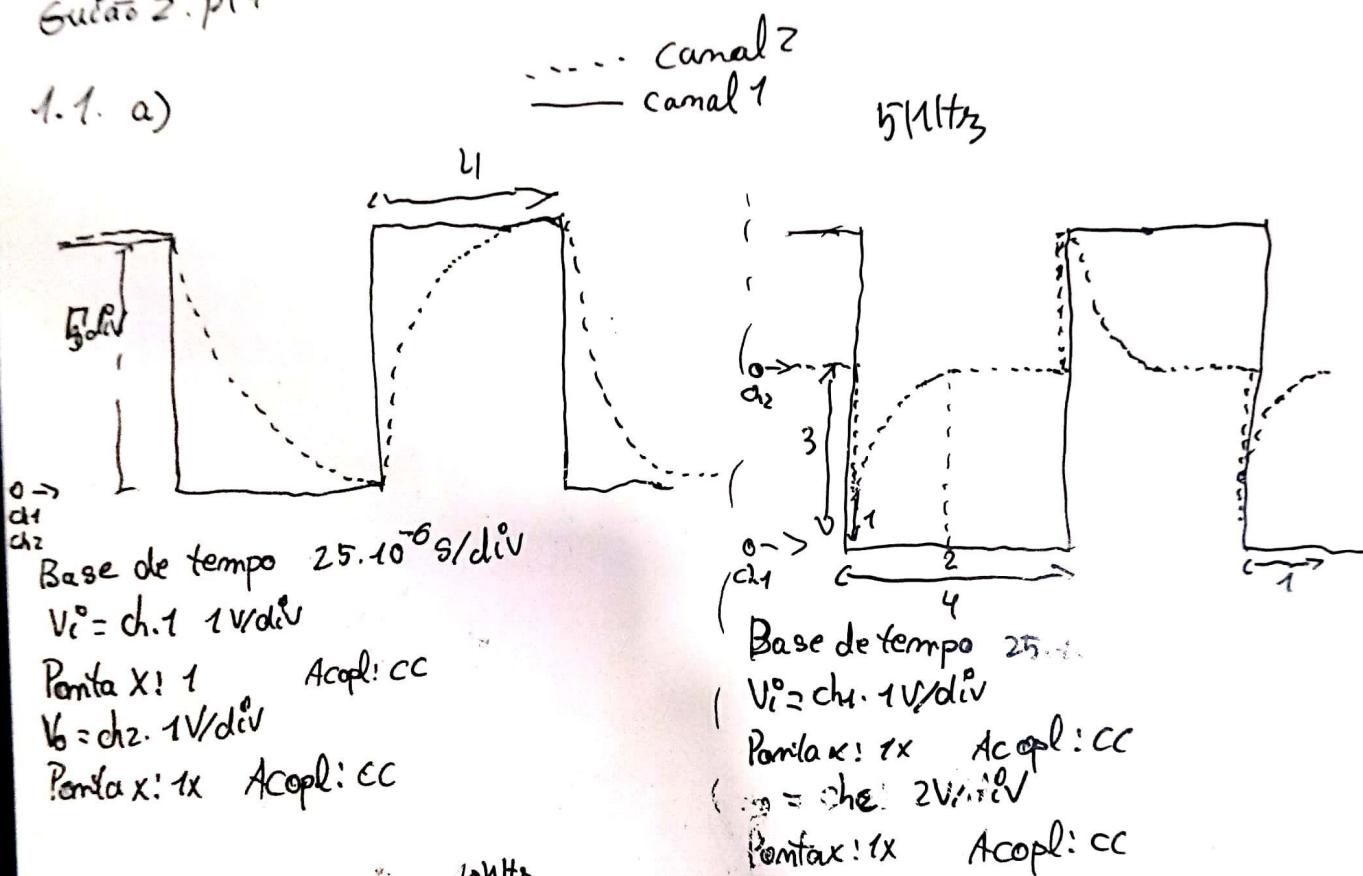

Física 1

Ex 3.

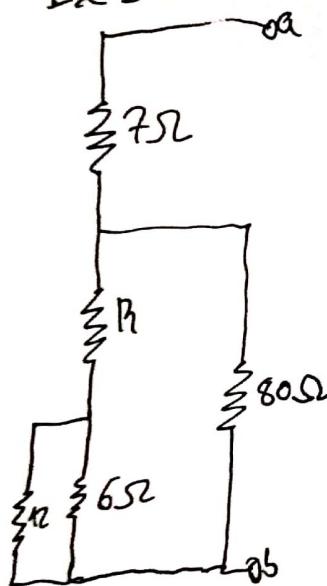

$$\text{Req}_1 = \frac{12 \times 6}{12 + 6} = 4 \Omega$$

$$\text{Req}_2 = 4 + R$$

$$\text{Req}_3 = \frac{(4+R)80}{80+4+R} = \frac{320+80R}{84+R}$$

$$\begin{aligned}\text{Req}_4 &= \frac{320+80R}{84+R} + 7 = \\ &= \frac{320+80R+7(84+R)}{84+R} = \\ &= \frac{908+87R}{84+R} = 23 \Omega\end{aligned}$$

$$\text{Caso } 908+87R = 23(84+R) \Rightarrow R = 16 \Omega$$

```

int max = 0
for(i=0; i < m; i++)
{
    if((m-i) == max) break;
    int rep = 1;
    for(j=i+1; j < m; j++)
    {
        Count++;
        if (array[i] == array[j])
            rep++;
        if (rep > max) max = rep;
    }
}
cout << max;
    
```


if (array[i] == array[j])
rep++
if (rep > max) max = rep;

	Salida Parte	Res	Ops	
1º seq	→ 1	10	10	resultado = n
2º seq.	→ 1	9	10	resultado = n-1
3º seq.	→ 1	8	19	- 3 $n+m-1$
4º seq.	→ 1	7	27	$n(3)+m-2$

$$A_c(m) = \frac{395}{11} = 35, 9 \approx 36 = 3n+6 - \frac{n(n+1)}{2}$$

SB
Página 1 (teórica)
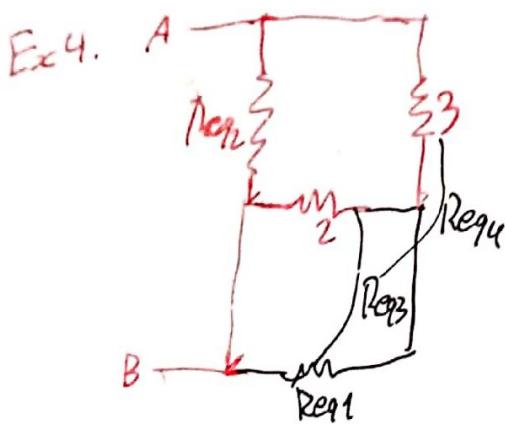
$$R_{eq1} = \frac{6 \times 3}{6+3} = 2\Omega$$



$$R_{eq2} = \frac{12 \times 6}{18} = 4\Omega$$


$$R_{eq3} = 2/12 = 1\Omega$$

$$R_{eq4} = 1+3 = 4\Omega$$

$$R_{AB} = 4//4 = 2\Omega //$$

Ex 5

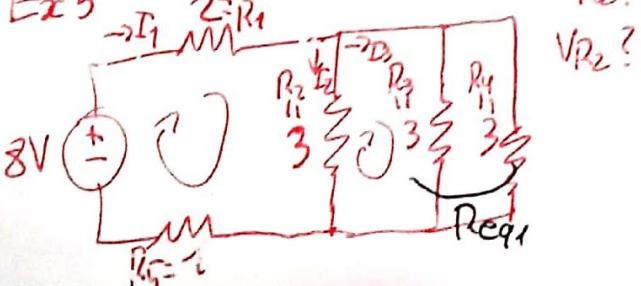
$$I_{R_2} ? \quad R_{eq1} = 3//3 = \frac{3}{2}$$



$$V_{R_2} ? \quad V_{R_2} = \frac{2}{3} \times 3 = 2V //$$

$$\begin{cases} -8 + 2I_1 + 3I_2 + I_3 = 0 \\ \frac{3}{2}I_3 - 3I_2 = 0 \\ I_1 = I_2 + I_3 \end{cases} \quad \begin{cases} 3I_1 + 3I_2 = 8 \\ -3I_2 + \frac{3}{2}I_3 = 0 \\ I_1 - I_2 - I_3 = 0 \end{cases} \quad \begin{cases} I_1 = 2 \\ I_2 = \frac{1}{3} \\ I_3 = \frac{4}{3} \end{cases}$$

Ex 6

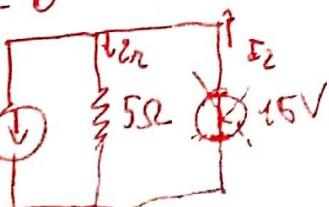

$$I_2 = 3A$$

$I_{ra} = 0A$, pq nãc passa nenhuma corrente pela resistência

$$I_{rb} \Rightarrow -15 + 5I_{rb} = 0 \Leftrightarrow I_{rb} = 3A$$


$$I_{rb} = I_{ra} + I_{rb} = 3A$$

$$I_r = I_{ra} + 3A = 6A$$

$$P = V \times I$$

$$= 15 \times 6 = 90W //$$

Ex 7.

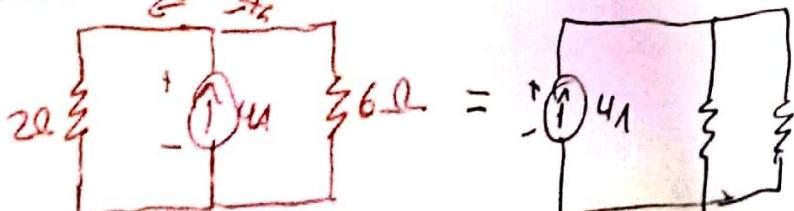


$$i_c = 4 \times \frac{6}{6+2} \quad (\text{divisor de corrente})$$

$$= 3A$$

$$P_6 = 14W //$$

(SE)

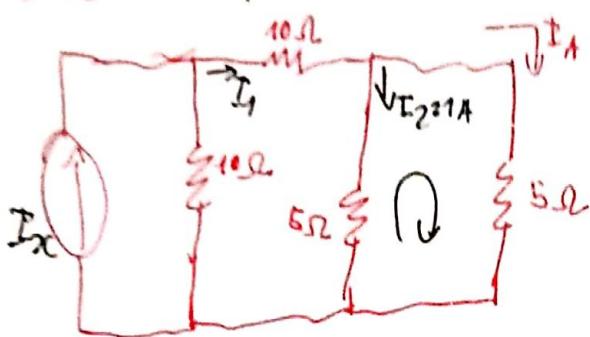Ex 8. I_x ?


$$5 - 5I_2 = 0 \Rightarrow I_2 = 1$$

$$I_1 = I_2 + 1 \Rightarrow I_1 = 2A$$

$$R_{FE} = (5/15) + 10 = 12,5\Omega$$

$$Z = I_x \frac{20}{10 + 12,5} \Rightarrow I_x = 4,5A$$

Ex 9.

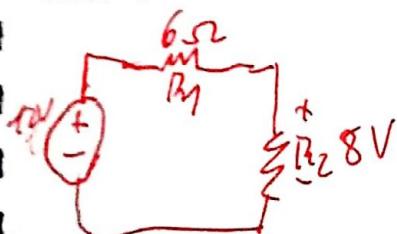


$$8 = 12 - \frac{R_2}{R_2 + R_1} \Rightarrow R_2 = 12\Omega$$

$$V = RI$$

$$I = \frac{V}{R}$$


$$I_2 = \frac{6}{12} = \frac{1}{2}A$$

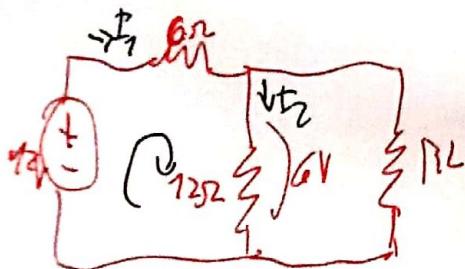

$$-12 + 6I_1 + 8 = 0 \Rightarrow I_1 = 1A$$

$$\frac{1}{2} = 1 \cdot \frac{R_L}{12 + R_L} \Rightarrow R_L = 12$$


Como a I divide-se em metade para I_2 logo as resistências são iguais

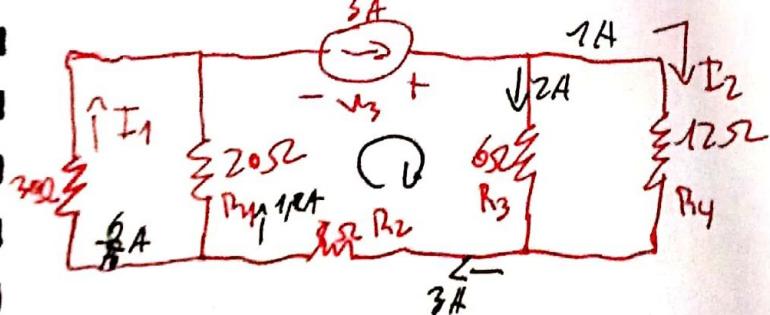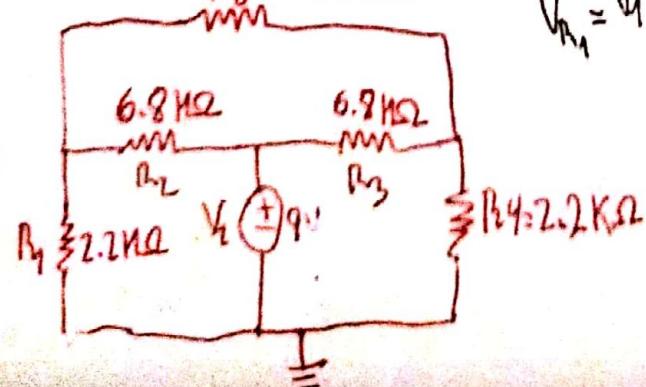Ex 10. I_1, I_2, V_3 ?

$$I_2 = 3 \cdot \frac{6}{18} \Rightarrow I_2 = 1A$$

$$I_1 = 3 \cdot \frac{20}{50} \Rightarrow I_1 = \frac{6}{5}A$$

$$-V_3 + 2 \cdot 6 + 8 \cdot 3 + 18 \cdot 20 = 0 \Rightarrow V_3 = 72V$$


Ex 11. $R_6 = 4,7\text{ k}\Omega$ 

$$V_{R_1} = V_1 \cdot \frac{R_1}{R_2 + R_1} = 2.2V$$

 I_5 ?

∞


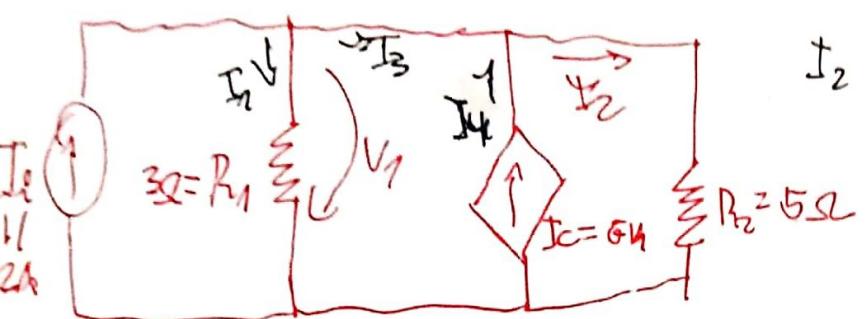
12. $V = RI$ $V_1?$ $G = 400 \text{ ms}$ $I_2 = ?$ $V_1 - V_C = V_2$



$$\begin{aligned} I_2 &= I_3 + I_C \\ &= I_3 + 0.4 \times 3(I_1 - I_3) \\ &= I_3 + 1.2(2 - I_3) \\ &= 2.4 - 0.2I_3 \end{aligned}$$

$$\begin{aligned} V_1 &= V_2 \\ (2 - I_3) \times 3 &= (2.4 - 0.2I_3) \times 5 \quad (2) \quad 6 - 3I_3 &= 12 - 10I_3 \Leftrightarrow -2I_3 = 6 \Leftrightarrow I_3 = -3A \\ V_1 &= (2 - (-3)) \times 3 = 15V \geq V_2 \quad I_2 = \frac{V_2}{R_2} = \frac{15}{5} = 3A \end{aligned}$$

13.

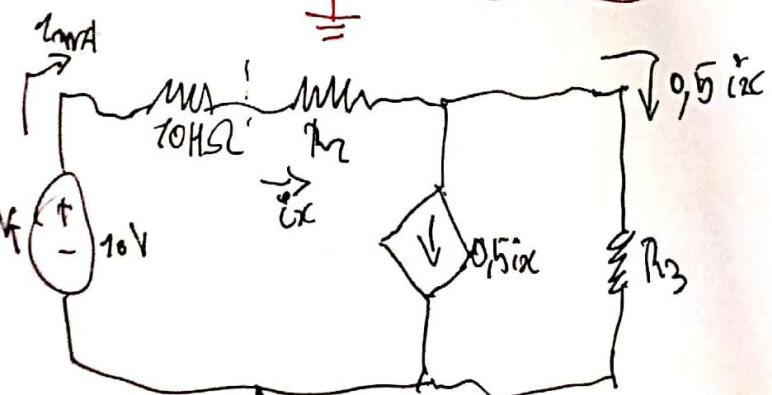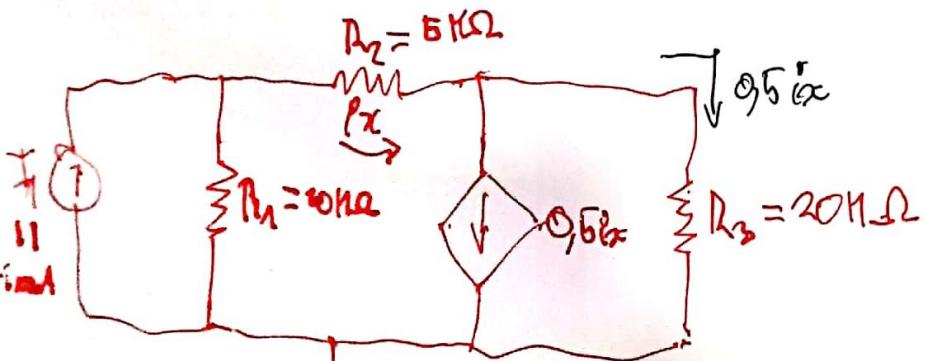

$$\begin{aligned} V_1 &= 10 \text{ mA} \times 10\text{k}\Omega \\ &= 10V \end{aligned}$$


$$10 = 10 \cdot 10^3 \cdot i_x + 5 \cdot 10^3 \cdot i_x + 0.5 \cdot i_x \cdot 20 \cdot 10^3$$

$$10 = i_x (10 + 5 + 10) \cdot 10^3$$


$$i_x = \frac{10}{25 \cdot 10^3} \Leftrightarrow i_x = 4 \cdot 10^{-4} A //$$

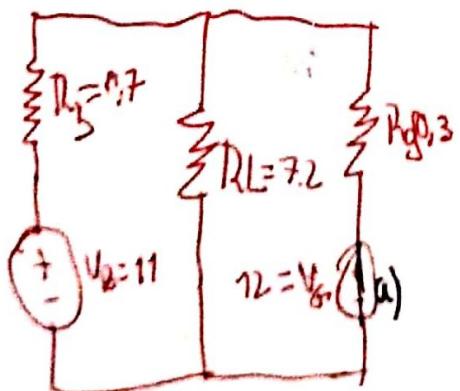14. a)

$$\begin{aligned} V_{RL} &=? \\ P_{RL} &=? \\ V_{RLa} &=? \end{aligned}$$



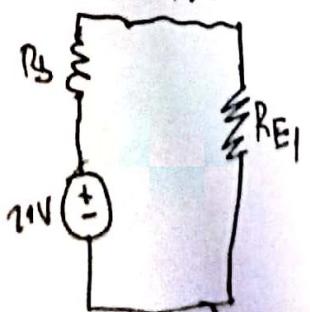
$$a) R_{E1} = \frac{7.2 \times 0.3}{7.5} = 0.288 \Omega$$



$$V_{RE1} = 11 \times \frac{R_E1}{R_E1 + R_L} = 3.2V$$

$$V_{RLa} = 3.2 \cdot \frac{R_L}{R_L + R_E1} = 3.078$$
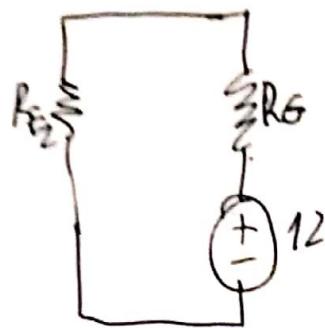
$$5) R_{E2} = \frac{7,2 \times 0,7}{3,9} = 0,645 \Omega$$



$$V_{R_{E2}} = 12 \times \frac{R_{E2}}{R_{E2} + R_G} = 8,2 \text{ V}$$


$$I_{R_{E2}} = \frac{8,2}{0,645 \Omega} = 12,84 \text{ A}$$

$$I_{RL} = 12 \times \frac{R_b}{R_b + R_L} = 2,14 \text{ A}$$


$$V_{RL} = 2,14 \times 7,2 = 15,208 \text{ V}$$

$$V_{RL} = V_{RLa} + V_{RLb} = 3,072 + 8,208 = 11,29 \text{ V}$$
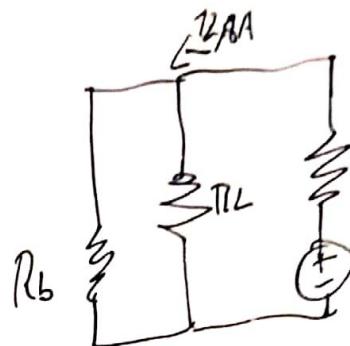
$$P = \frac{V_{RL}^2}{R_L} = 17,69 \text{ W}$$



15.

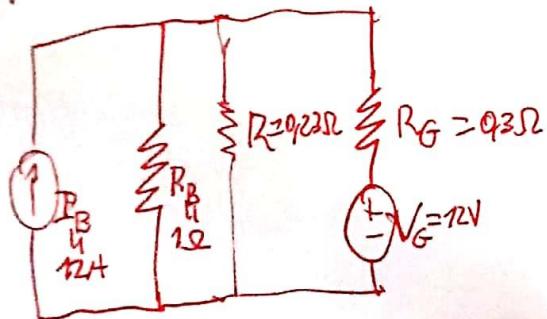


$$R_{E1} = \frac{R_B R_G}{R_B + R_G} = 0,13 \Omega$$

$$I_{R_{E1}} = 12 \times \frac{R_B}{R_B + R_{E1}} = 10,62 \text{ A}$$



$$V_{R1} = I_R \times R = 1,38 \text{ V}$$

a)

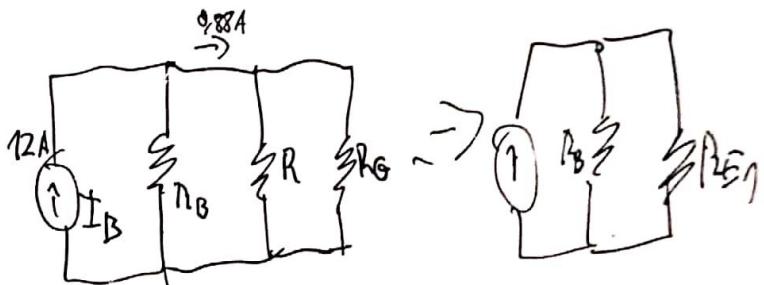

$$I_R = 10,62 \times \frac{R_G}{R + R_G} = 6 \text{ A}$$

b)

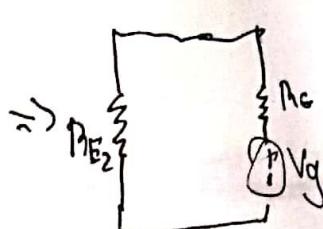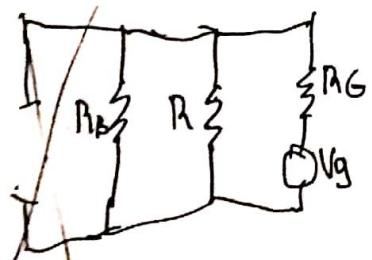

$$V_{R_{E2}} = V_g \times \frac{R_{E2}}{R_{E2} + R_g} = 4,61 \text{ V}$$


$$R_{E2} = \frac{R \times R_B}{R + R_B} = 0,19$$

$$I_{R_{E2}} = \frac{4,61}{R_{E2}} = 24,25 \text{ A}$$

$$I_R = I_{R_{E2}} \times \frac{R_B}{R + R_B} = 19,72 \text{ A}$$

$$V_{R_2} = 0,23 \times 19,72 = 4,53 \text{ V}$$



$$V_R = 4,53 + 1,38 = 5,91 \text{ V}$$

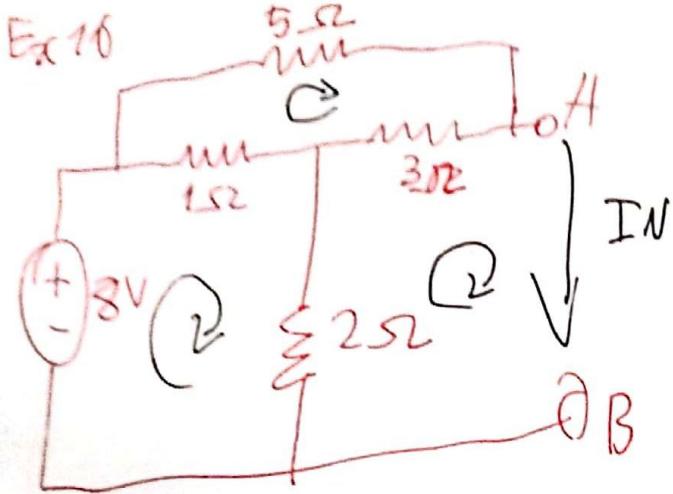

Ficha 2.

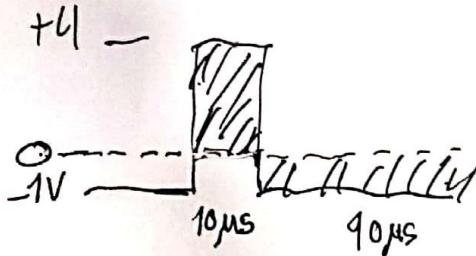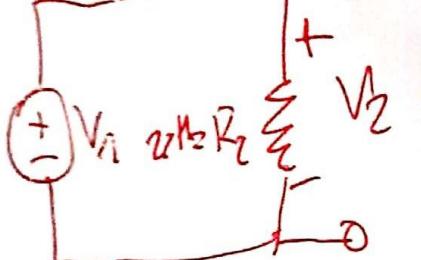1.

$$R_1 = 22\text{ M}\Omega \quad V_2 = V_1 \times \frac{22.10^3}{44.10^3} \Leftrightarrow V_2 = \frac{V_1}{2}$$



$$T = 100 \cdot 10^{-6} \text{ s}$$

$$V_{pp} = 5 \text{ V}$$

$$V_m = 4 \times 0,1 - 1 \times 0,9 = -0,5 \text{ V}$$

$$V_{ef}^2 = \frac{1}{T} \int_0^T V(t)^2 dt = \frac{1}{T} \left(\int_0^{10\mu\text{s}} 4^2 dt + \int_{10\mu\text{s}}^{100\mu\text{s}} (-1)^2 dt \right) = \frac{1}{100 \cdot 10^{-6}} (16 \cdot 10^{-4} + 0,9 \cdot 10^{-4}) \Leftrightarrow V_{ef} = \sqrt{25} \text{ V}$$

$$\delta (\text{duty-cycle}) = \frac{10 \cdot 10^{-6}}{100 \cdot 10^{-6}} \approx 10\%$$

Vrms

2.

$$V_{pp} = 3 \text{ V}$$

$$V_m = 1,5 \text{ V}$$

3. $V_{pp} = 300 \text{ V}$

$$V_{ef} = \frac{V_{max}}{\sqrt{2}} = \frac{150}{\sqrt{2}} = 106 \text{ Vrms},$$

$$\cos(\omega t) \rightarrow \text{pico positivo} \rightarrow x = 0$$

$$200\pi t - 36^\circ = 0 \Rightarrow 200\pi t - 0,2\pi = 0$$

$$\Leftrightarrow t = \frac{0,2\pi}{200\pi} \Leftrightarrow t_{\max} = 1 \cdot 10^{-3} \text{ s}$$

C.A	$180 - \pi$
$36 - x$	$x = 0,2\pi$

$$f = 100 \text{ Hz}$$


$$T = \frac{1}{100} = 10 \text{ ms}$$

$$W = 200 \cdot \pi \approx 628 \text{ rad/s},$$

$$P = \frac{V^2}{R} = \frac{106^2}{50} = 225 \text{ W},$$


Ficha 1.

17.

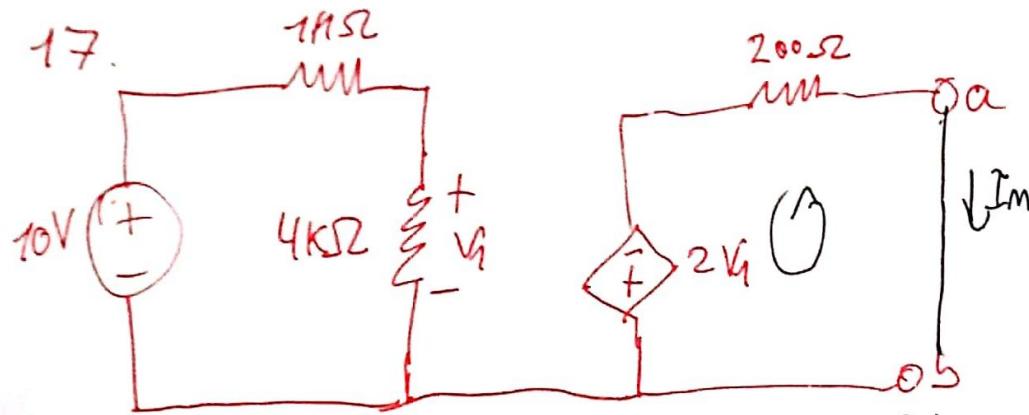


$$V_1 = 10 - \frac{4 \cdot 10^3}{5 \cdot 10^3} = 8 \text{ V}$$
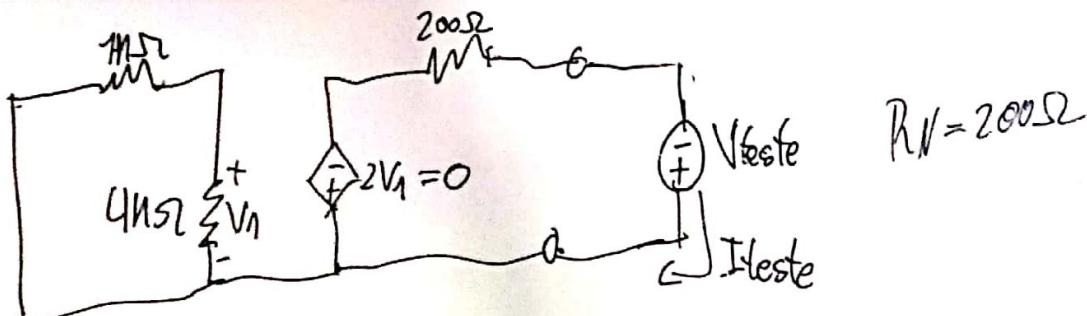
$$I_N = -\frac{2 \cdot 8}{200} = -80 \cdot 10^{-3} \text{ A}$$




$$V_1 = 0$$

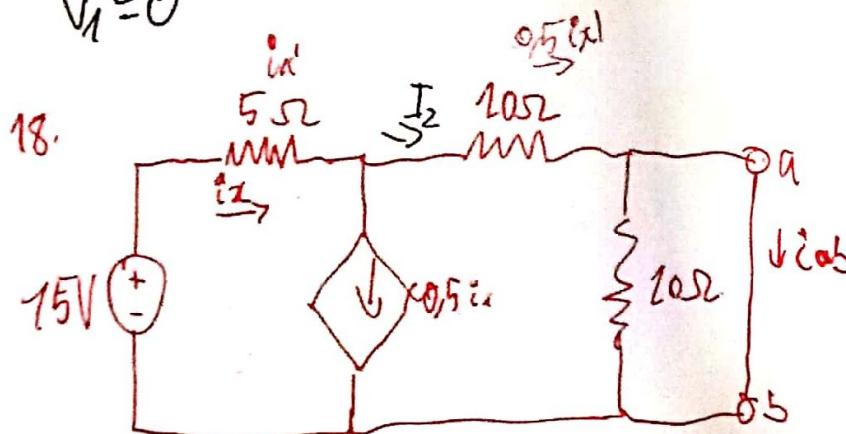

$$\begin{cases} I_x = 0,5 I_x + I_2 \\ 15 = 5 I_x + 20 I_2 \end{cases} \Leftrightarrow \begin{cases} \frac{I_x}{2} = I_2 \\ I_2 = \frac{15 - 5 I_x}{20} \end{cases} \Leftrightarrow \begin{cases} \frac{I_x}{2} = \frac{15}{20} - \frac{I_x}{4} \\ I_2 = \frac{15}{20} - \frac{I_x}{4} \end{cases} \Leftrightarrow \begin{cases} \frac{3 I_x}{4} = \frac{15}{4} \\ - \quad - \end{cases} \begin{cases} I_x = 1,5 \\ I_2 = 0,5 \end{cases}$$

$$V_f = 10 \cdot 0,5 = 5 \text{ V}_f$$

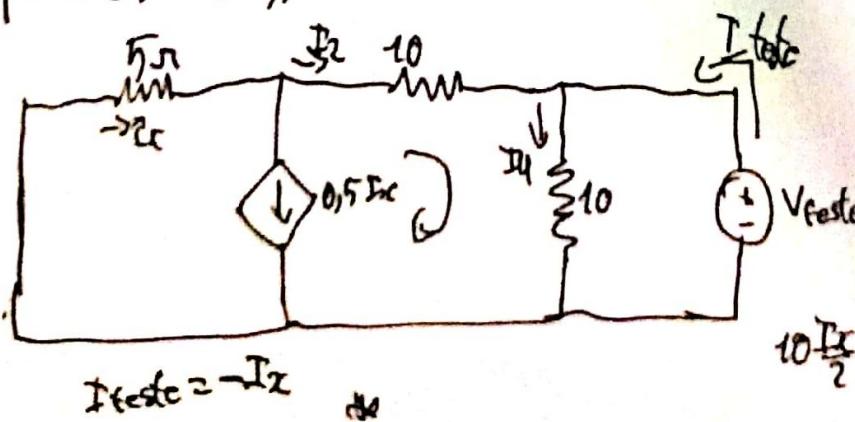


$$I_x = 0,5 I_x + I_2 \Leftrightarrow I_2 = \frac{I_x}{2}$$

$$I_2 + I_{teste} = I_4$$

$$\Leftrightarrow I_{teste} = I_4 - \frac{I_x}{2}$$

$$10 \frac{I_x}{2} + 10 I_4 - \frac{I_x}{2} = 0 \Leftrightarrow I_4 = -\frac{I_x}{2}$$

∞

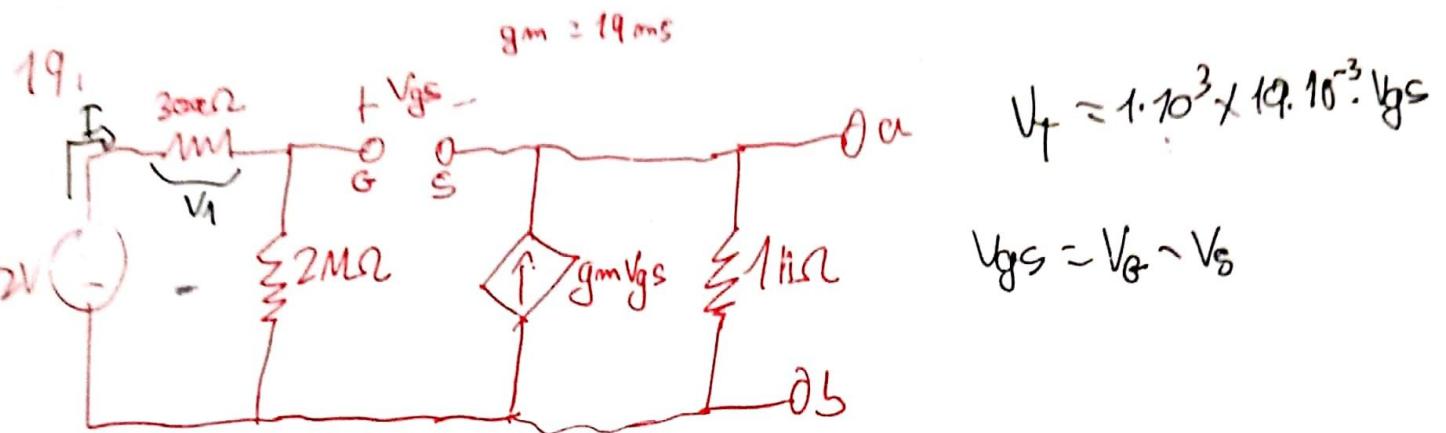

$$2 = 300I + 2 \cdot 10^6 I \Rightarrow I = \frac{2}{2000 \cdot 300} \text{ A}$$

$$1 \cdot 10^3 \times 19 \cdot 10^{-3} (V_B - V_S) = V_D \Rightarrow$$

$$V_D = \frac{2}{2000 \cdot 300} \times 300 \approx 3 \cdot 10^{-4} \text{ V}$$


$$\Rightarrow 1 \cdot 10^3 \times 19 \cdot 10^{-3} \times 1,9997 = 20 \text{ V} \Rightarrow$$

$$\Rightarrow V_S = 1,8997 \text{ V}$$

$$V_G = 2 - 3 \cdot 10^{-4} \approx 1,9997 \text{ V} \approx 2 \text{ V}$$

$$V_{gs} = 0,1 \text{ V}$$

$$V_T = 19 \text{ V}$$

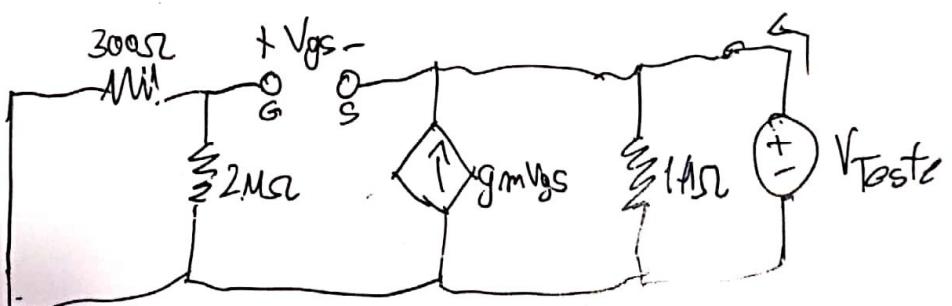

$$V_G = 0$$

$$V_S = 1 \cdot 10^3 \times (I_{\text{teste}} + 19 \cdot 10^{-3} (-V_S)) \Rightarrow V_S = 1 \cdot 10^3 I_{\text{teste}} - 19 V_S \Rightarrow V_S = 50 I_{\text{teste}}$$

$$V_{\text{teste}} = 1 \cdot 10^3 \times (0,019 \times (-50 I_{\text{teste}}) + I_{\text{teste}}) \Rightarrow V_{\text{teste}} = 50 I_{\text{teste}}$$


$$R_T = \frac{V_{\text{teste}}}{I_{\text{teste}}} = \frac{50 I_{\text{teste}}}{I_{\text{teste}}} = 50 \Omega$$

$$c: I = C \frac{dV}{dt}$$

$$\beta \neq V = L \frac{dI}{dt}$$

Ficha 2.

4.?



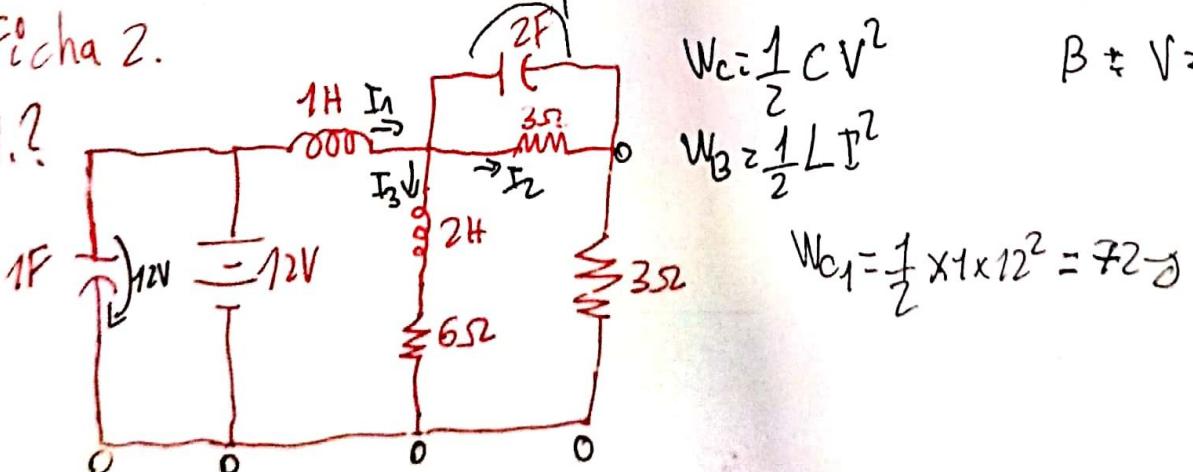


$$W_C = \frac{1}{2} C V^2$$

$$W_R = \frac{1}{2} L I^2$$

$$W_{C1} = \frac{1}{2} \times 1 \times 12^2 = 72 \text{ J}$$

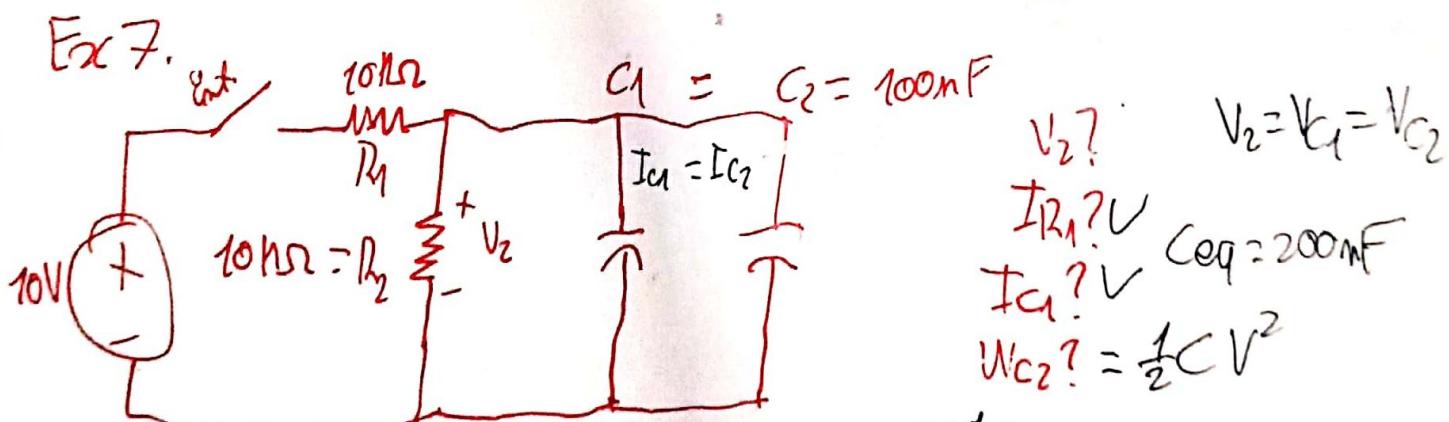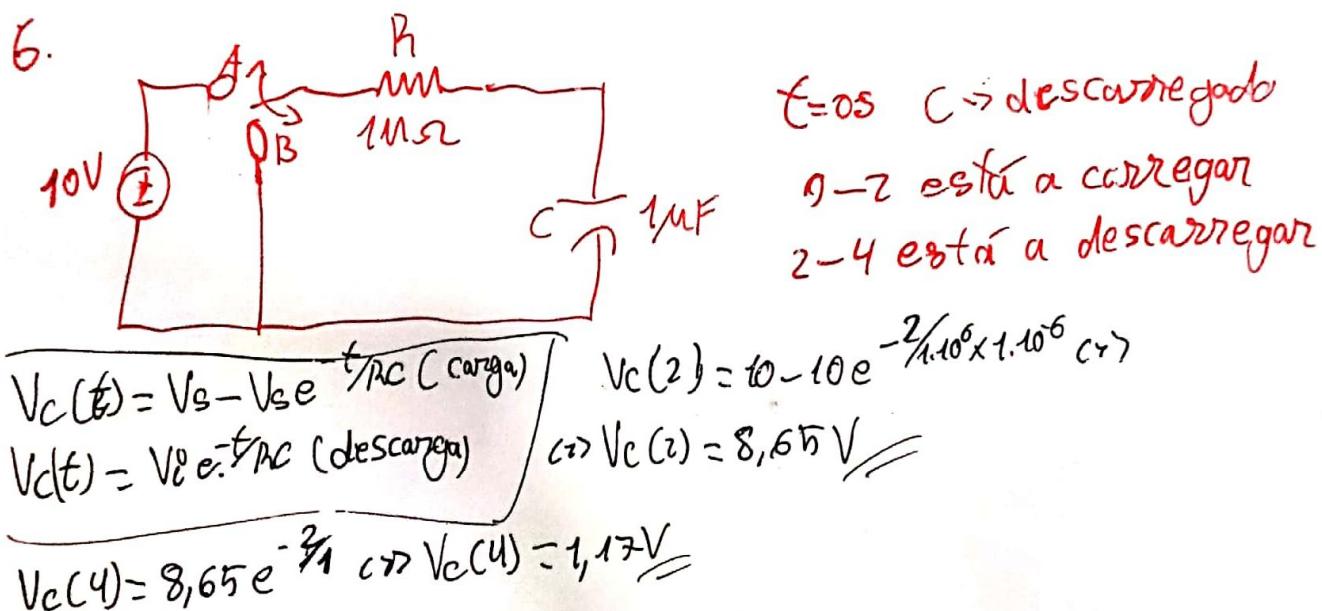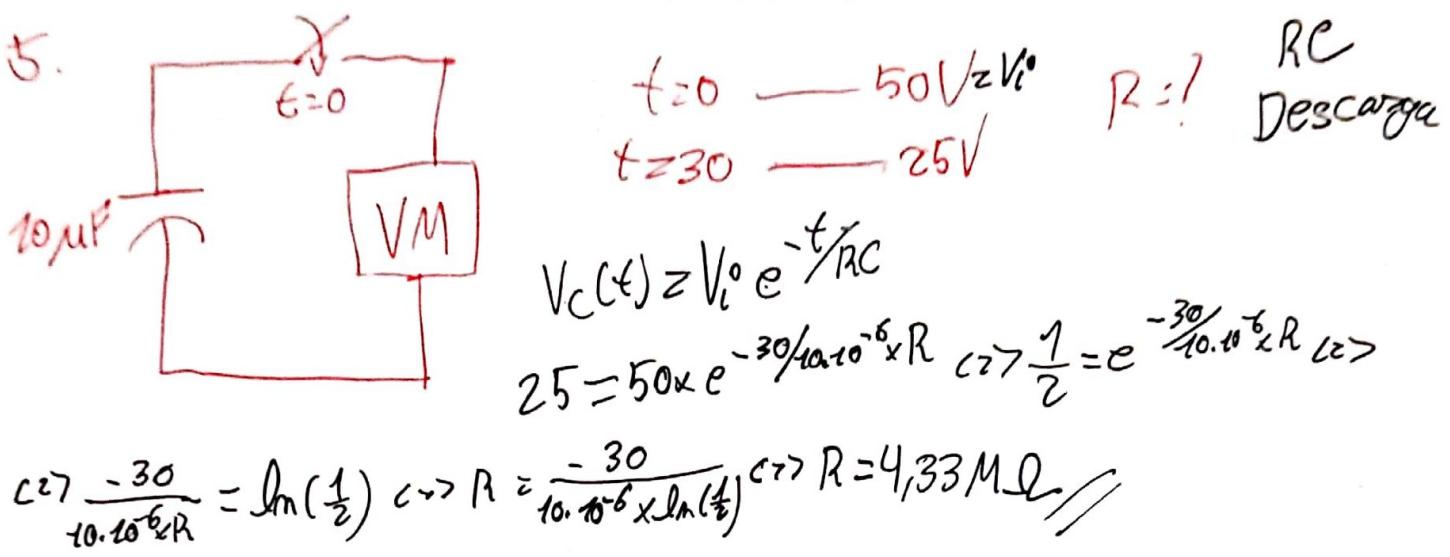Regione permanente $\rightarrow I_C = 0$ (circuito aberto)
 $t > 5 \text{ s}$ $\hookrightarrow V_B = 0$ (curto-circuito)




$$t=0S \quad V_2 = 10 \times \frac{10 \cdot 10^3}{20 \cdot 10^3} = 5V \quad V_2(0,001) = 5 \times e^{-0,001} = 3,03V ? 3,16$$



$$I_{M1} = \frac{10 - 3,16}{10 \cdot 10^3} = 684 \cdot 10^{-6} = 684 \mu A$$

$$684 \cdot 10^{-6} = 257 \frac{3,16}{10 \cdot 10^3} \Leftrightarrow I = 368 \cdot 10^{-6} = I_{C1} = 368 \mu A$$
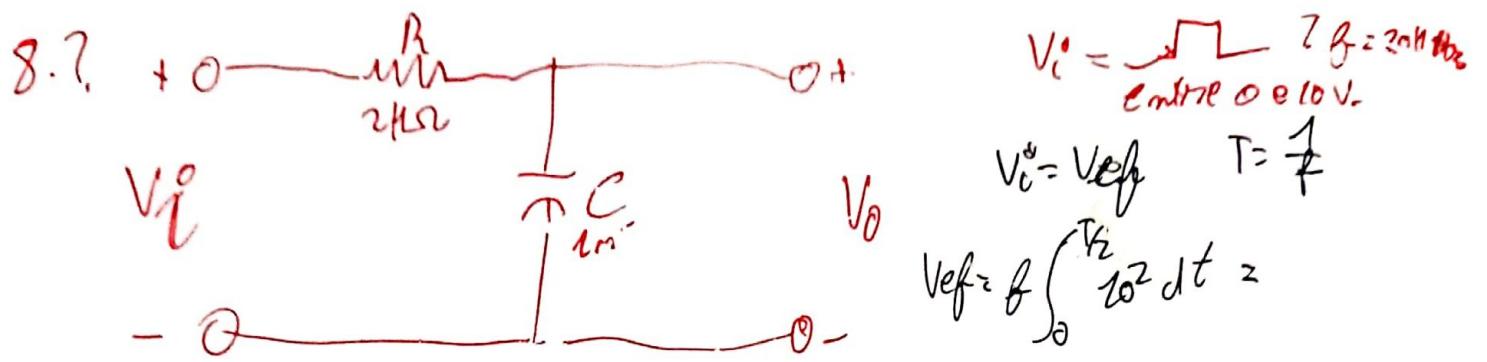
$$V_{C2} = \frac{1}{2} 100 \cdot 10^{-9} \times (3,16)^2 = 5 \cdot 10^{-9} V = 0,5 \mu V$$


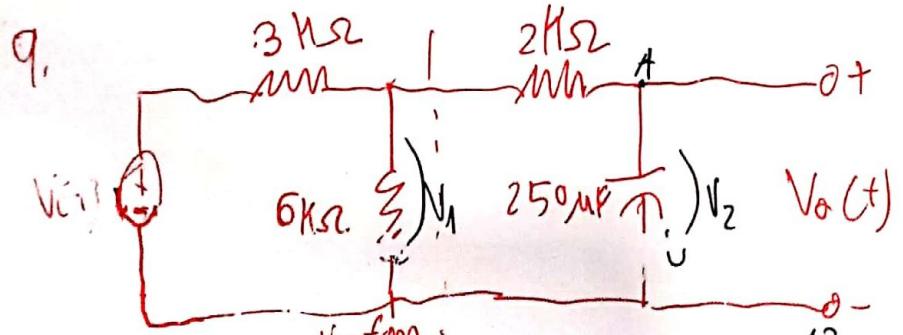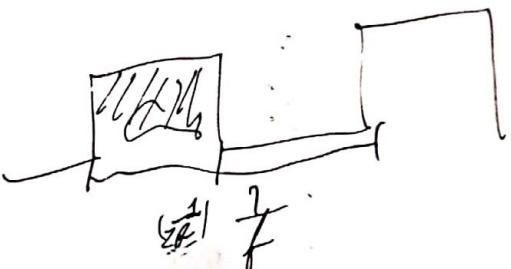
$$V_o = V_i^o \times \frac{Z_C}{Z_R + Z_C} =$$







$$V_o(1) = V_2$$

Larga ($0-1$) descarga ($1-2$)

$$V_2(1) = V_{AC(0-1)} \times \left(1 - e^{-\frac{t}{RC}}\right)$$

$$I_N = \frac{12}{3 H}$$

$$R_N = (3/6) = 2 H$$

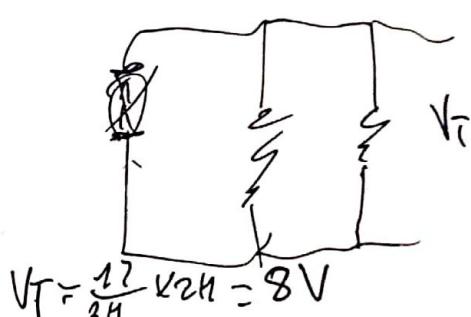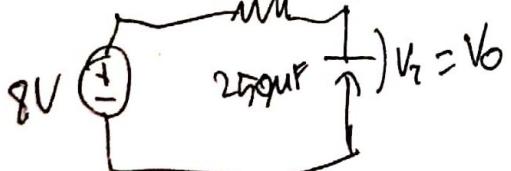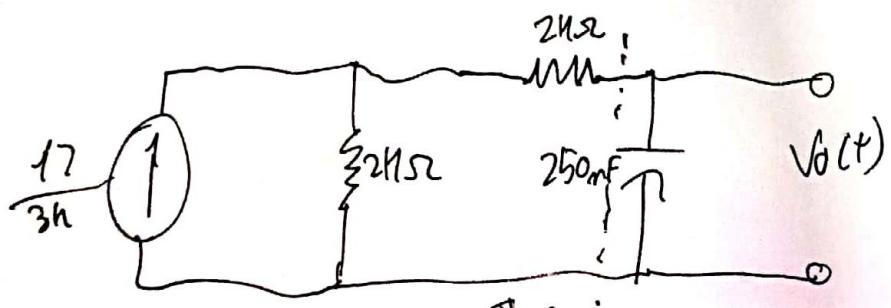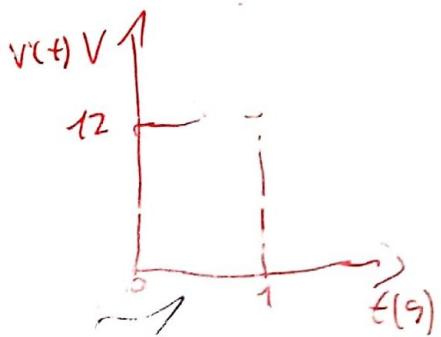

$$V_o(1) = 8 \times \left(1 - e^{-\frac{1}{4 \cdot 10^3 \times 250 \cdot 10^{-6}}} \right) \approx 5,1 V$$

$$V_o(2) > 5,1 \times e^{-\frac{1}{4 \cdot 10^3}} = 1,4 V$$

Trabalho Prático 2º PT1

$$f_C = \frac{1}{2\pi R C} \approx 16 \text{ Hz}$$

$$V_0 = V_i \frac{Z_C}{Z_R + Z_C} \Rightarrow \frac{V_0}{V_i} = \frac{Z_C}{Z_R + Z_C}$$

$$Z_C = \frac{1}{j\omega C} \xrightarrow{R} R = \frac{1}{\sqrt{1 + (\frac{\omega}{f_C})^2}}$$

$$\frac{1}{j\omega C} = \frac{1}{j\omega R + 1} = \frac{1}{j\omega R(1 + \frac{1}{j\omega R})} = \frac{1}{j\omega R + 1}$$

$$\angle H(f) = -\arctan\left(\frac{1}{16}\right) = 3,6^\circ$$

$$V_0 = V_i \frac{Z_R}{Z_R + Z_C}$$


$$H(f) = \frac{V_0}{V_i} = \frac{j(\frac{\omega}{f_C})}{1 + j(\frac{\omega}{f_C})}$$

$$|H(f)| = \frac{6\mu\text{e}}{\sqrt{1 + (\frac{\omega}{f_C})^2}} \approx 0,66$$

$$\angle H(f) = 90^\circ - \omega \tan\left(\frac{1}{f_C}\right) \approx 86,4^\circ$$


Ficha 2

4.

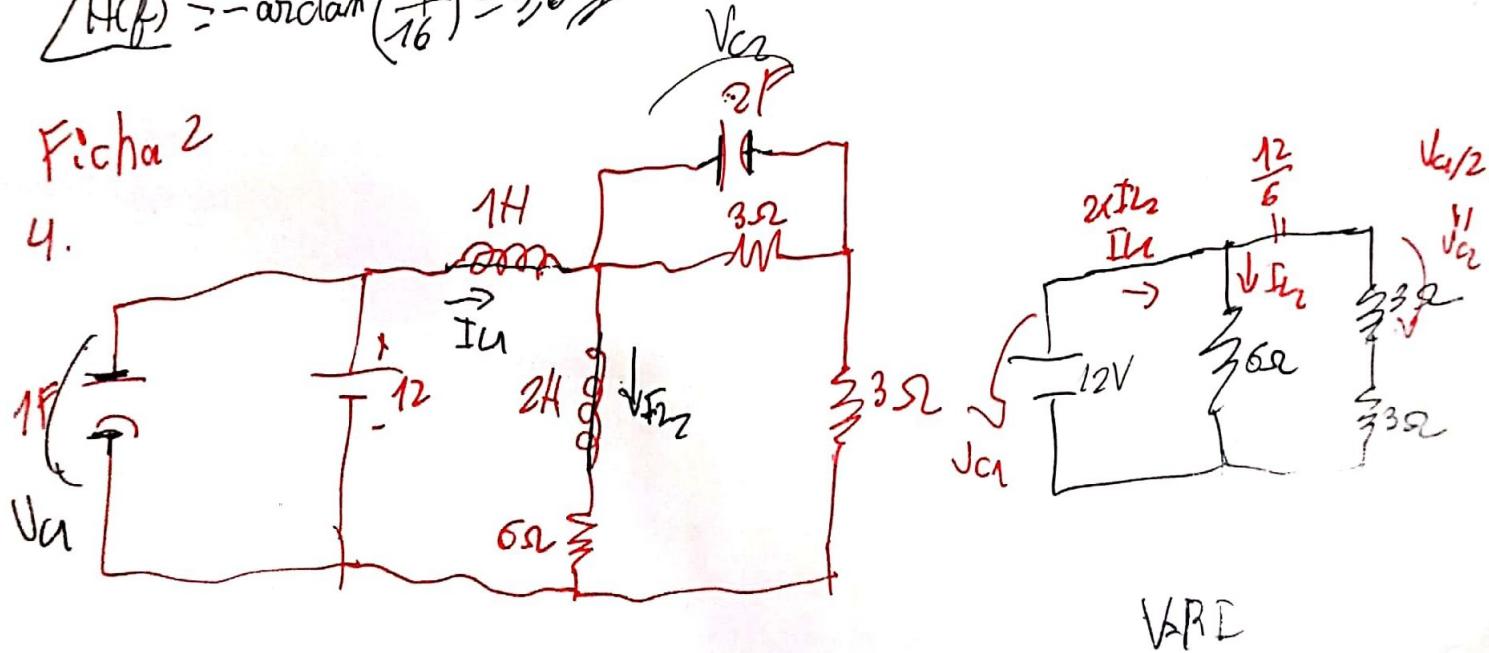

VRI

10?

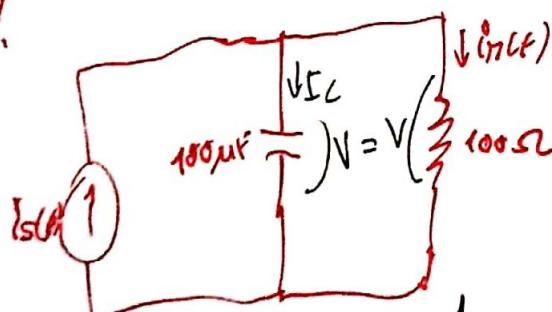

$$i_s(t) = 1 \cos(200\pi t)$$

$$i_s = 1 \angle 0^\circ$$

$$i_{eq}(t) = i_s(t) \times \frac{Z_C}{Z_C + Z_R}$$

$$i_s = \frac{V_{eq}}{R}$$

$$i_s = I_C + I_R$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 200\pi \times 100 \cdot 10^{-6}} = \frac{1}{2\pi^2 \times 10^4} = -j15,9 \Omega$$


$$\frac{1}{Z_R} = \frac{1}{1 + 2\pi f D} = \frac{1}{1 + 2\pi \times 10 \times 10^{-3}} = 0,064 \angle 81^\circ \Omega$$

$$\arctan\left(\frac{2\pi \times 10^2}{0,064}\right) \approx 81^\circ$$

$$V_{eq} = 1 \angle 0^\circ \times 0,064 \angle 81^\circ$$

∞

11.? rés mal.

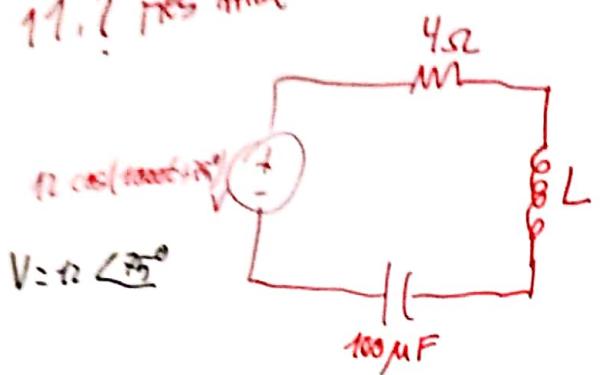


$$Z_L = jWL = j \times 1000 \times L \angle 90^\circ \quad \Phi = \tan^{-1} \left(\frac{Imaginary}{Real} \right)$$

$$Z_C = -j \times \frac{1}{1000 \times 100 \cdot 10^{-6}} = -j \times 10 \text{ } \Omega$$

$$\begin{aligned} Z_{eq} &= 4 + j \times 1000 \times L - 10j \\ &= 4 + j(1000L - 10) \end{aligned}$$

$$75^\circ = \arctg \left(\frac{1000L - 10}{4} \right) \Rightarrow \operatorname{tg} 75^\circ \times 4 = 1000L - 10 \Rightarrow L = \frac{(875 \times 4) + 10}{1000} \Rightarrow L = 24,9 \text{ mH?}$$

12.

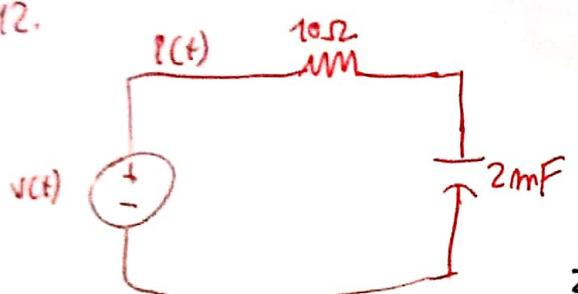

$$V(t) = 25 \cos(\omega t) = 25 \angle 0^\circ$$


$$Z_C = \frac{1}{W \times 2 \cdot 10^3 \times j} = -j \times \frac{1}{W} \times 500 \text{ } \Omega$$

$$\begin{aligned} Z_{eq} &= 10 - \frac{500}{W} j = 10 - \frac{250}{\pi f} j = \sqrt{10^2 + \left(\frac{250}{\pi f} \right)^2} \\ &\approx \sqrt{100 + \left(\frac{62500}{\pi^2 f^2} \right)} \end{aligned}$$

$$25 \angle 0^\circ = 2 \times \sqrt{100 + \frac{62500}{\pi^2 f^2}} \quad \operatorname{arctg} \left(\frac{-500}{10 \times 2500} \right) \Rightarrow$$

$$\Rightarrow 12,5^2 = 100 + \frac{62500}{\pi^2 f^2} \Rightarrow \frac{12,5^2 - 100}{62500} = \frac{1}{\pi^2 f^2} \Rightarrow f = \sqrt{\frac{62500}{(12,5^2 - 100)\pi^2}} \approx 10,6 \text{ Hz}$$

13.?

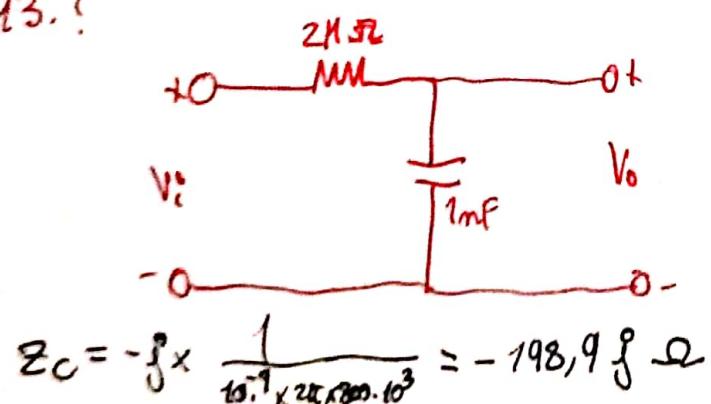

$$V_i = 14,1 \cos(2\pi \times 800 \cdot 10^3 t)$$

$$V_{eff} = ?$$

$$I = \frac{14,1 \angle 0^\circ}{2 \cdot 10^3 \angle 57^\circ} = 7 \cdot 10^{-4} \angle 5,7^\circ \text{ A}$$

$$\begin{aligned} V_o &= 7 \cdot 10^{-4} \angle 57^\circ \times (-198,9 \angle -90^\circ) \\ &= 9,14 \angle -84,3^\circ \end{aligned}$$

c. A.

$$\begin{aligned} \sqrt{(2 \cdot 10^3)^2 + (198,9)^2} &= 2,01 \cdot 10^3 \\ \operatorname{arctg} \left(\frac{-198,9}{2 \cdot 10^3} \right) &= 5,7^\circ \end{aligned}$$